


# **Pipelined RISC-V Processor**

# Pipelined RISC-V Processor


- **Temporal parallelism**
- Divide single-cycle processor into **5 stages**:
  - Fetch
  - Decode
  - Execute
  - Memory
  - Writeback
- Add **pipeline registers** between stages

# Single-Cycle vs. Pipelined Processor


## Single-Cycle

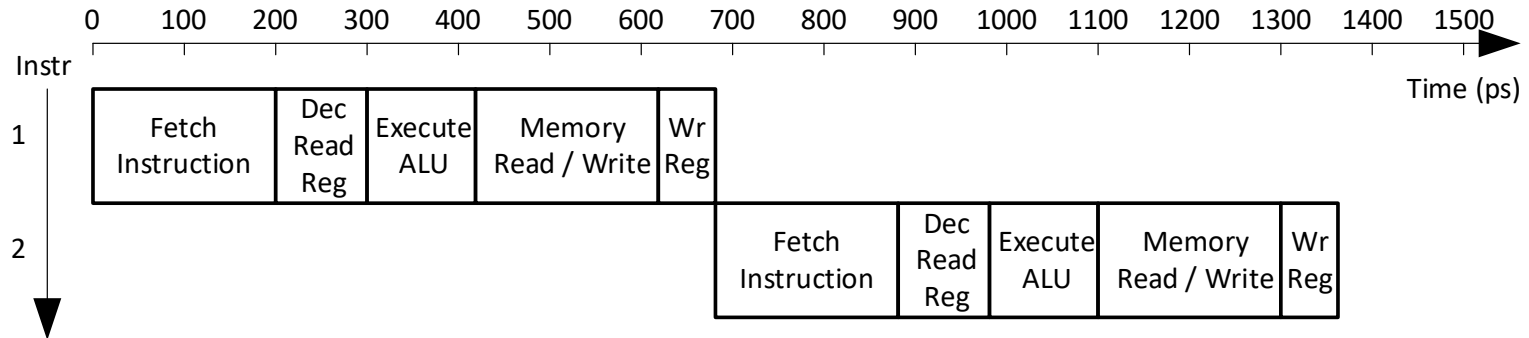



## Pipelined

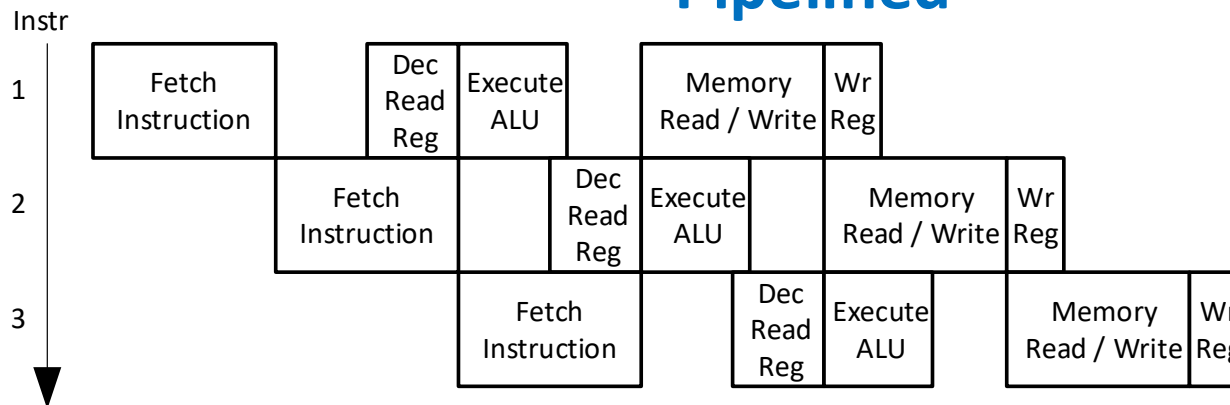

# Pipelined Processor Abstraction

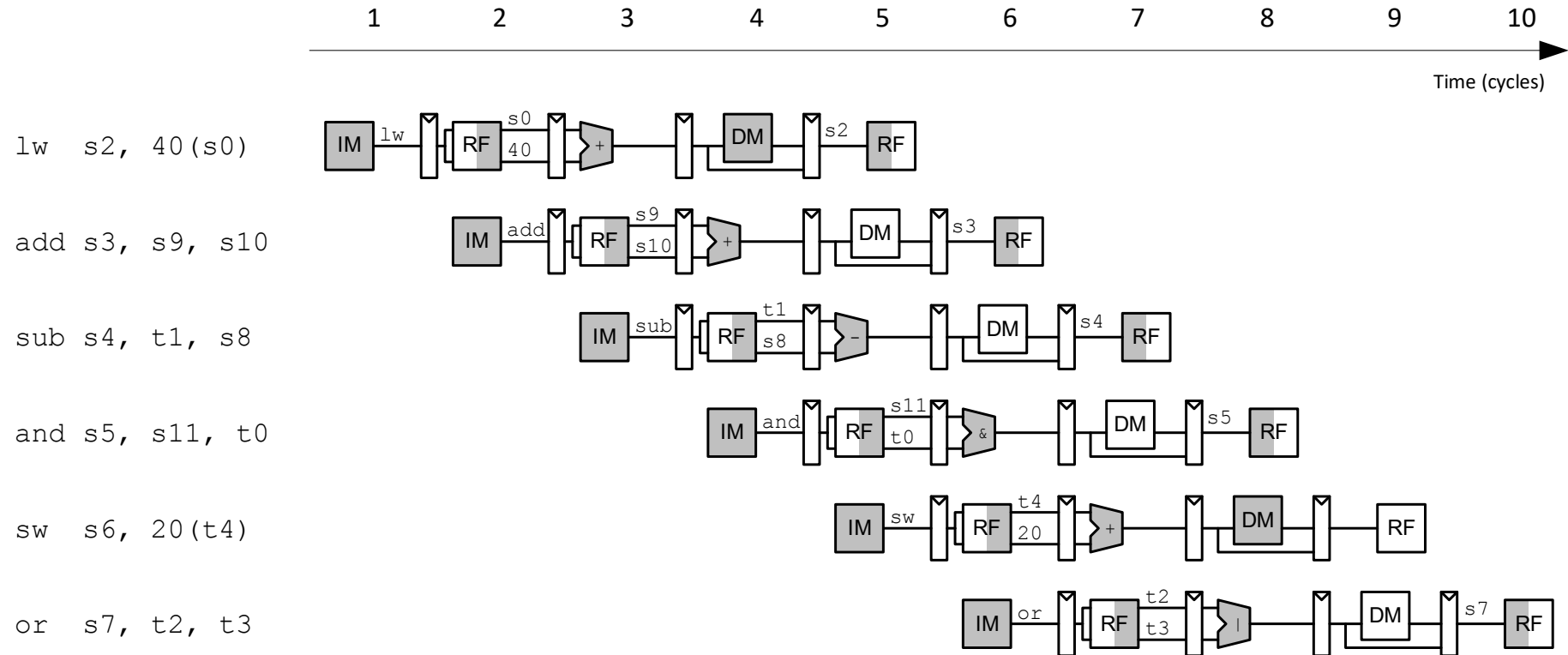


# Single-Cycle & Pipelined Datapaths

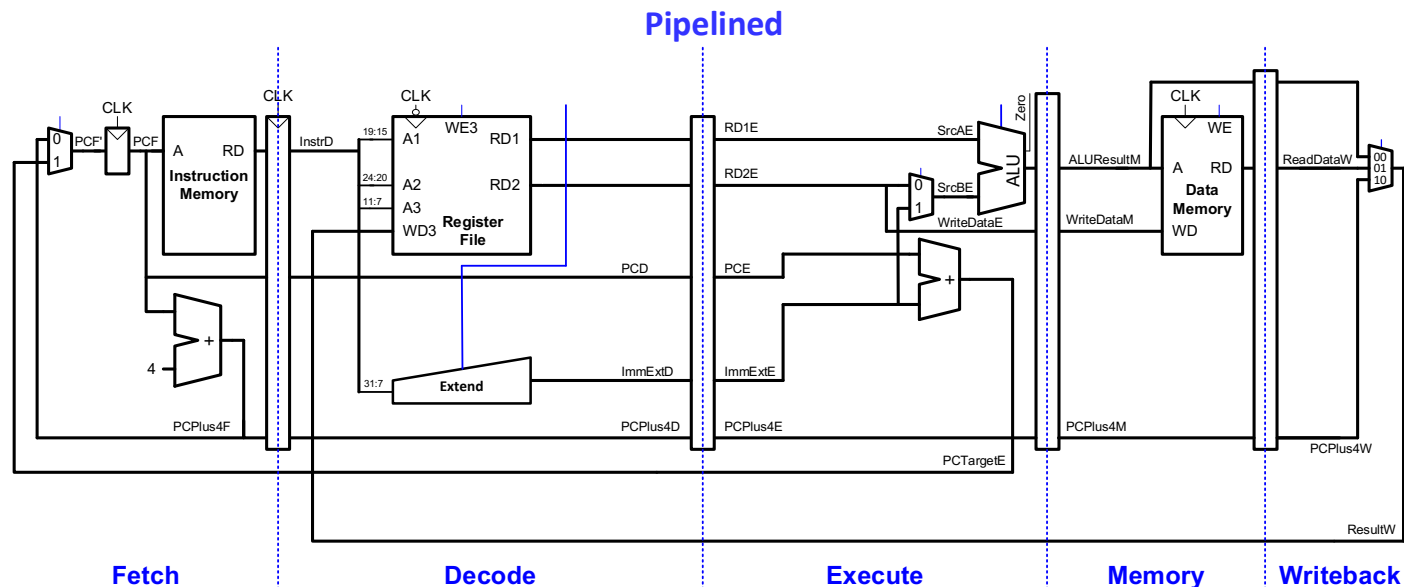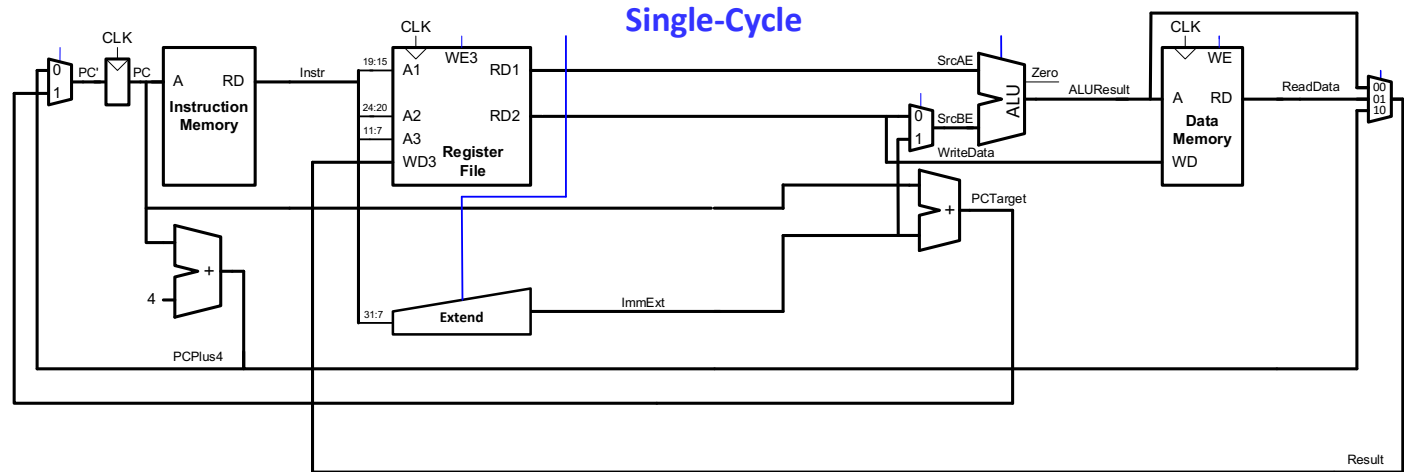


Signals in Pipelined Processor are appended with first letter of stage (i.e., PCF, PCD, PCE).

# Corrected Pipelined Datapath

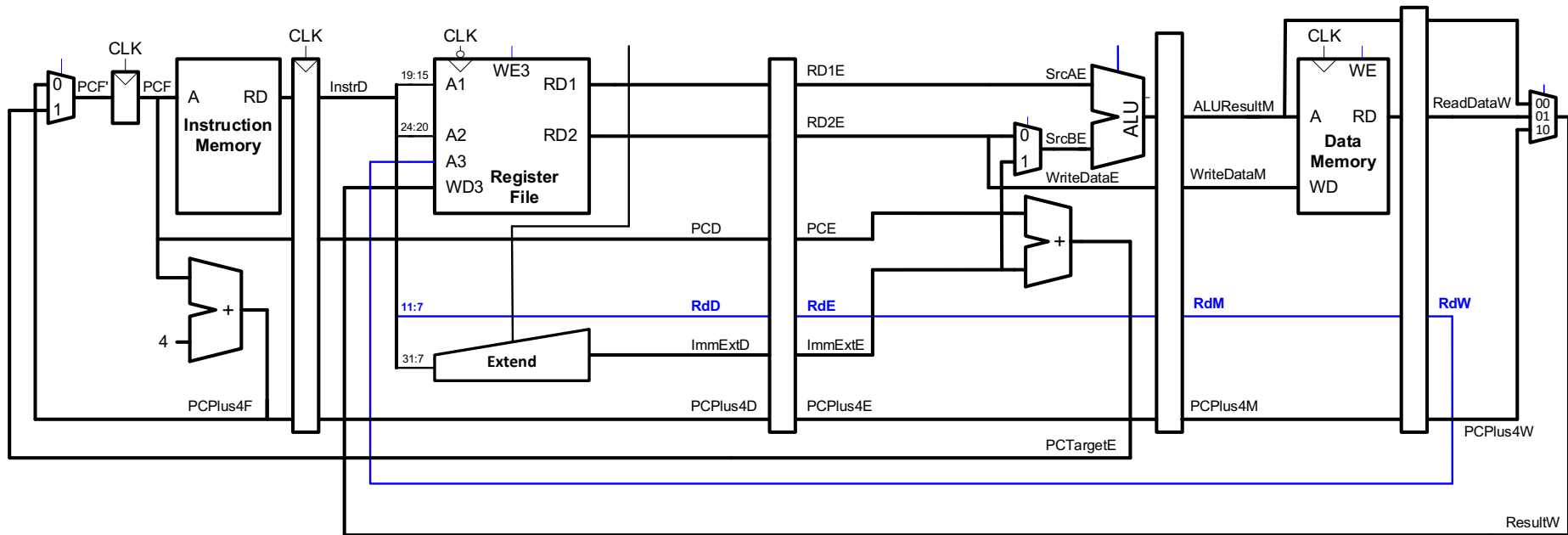

- ***Rd*** must arrive at same time as ***Result***
- Register file written on **falling edge** of *CLK*

# Pipelined Processor with Control

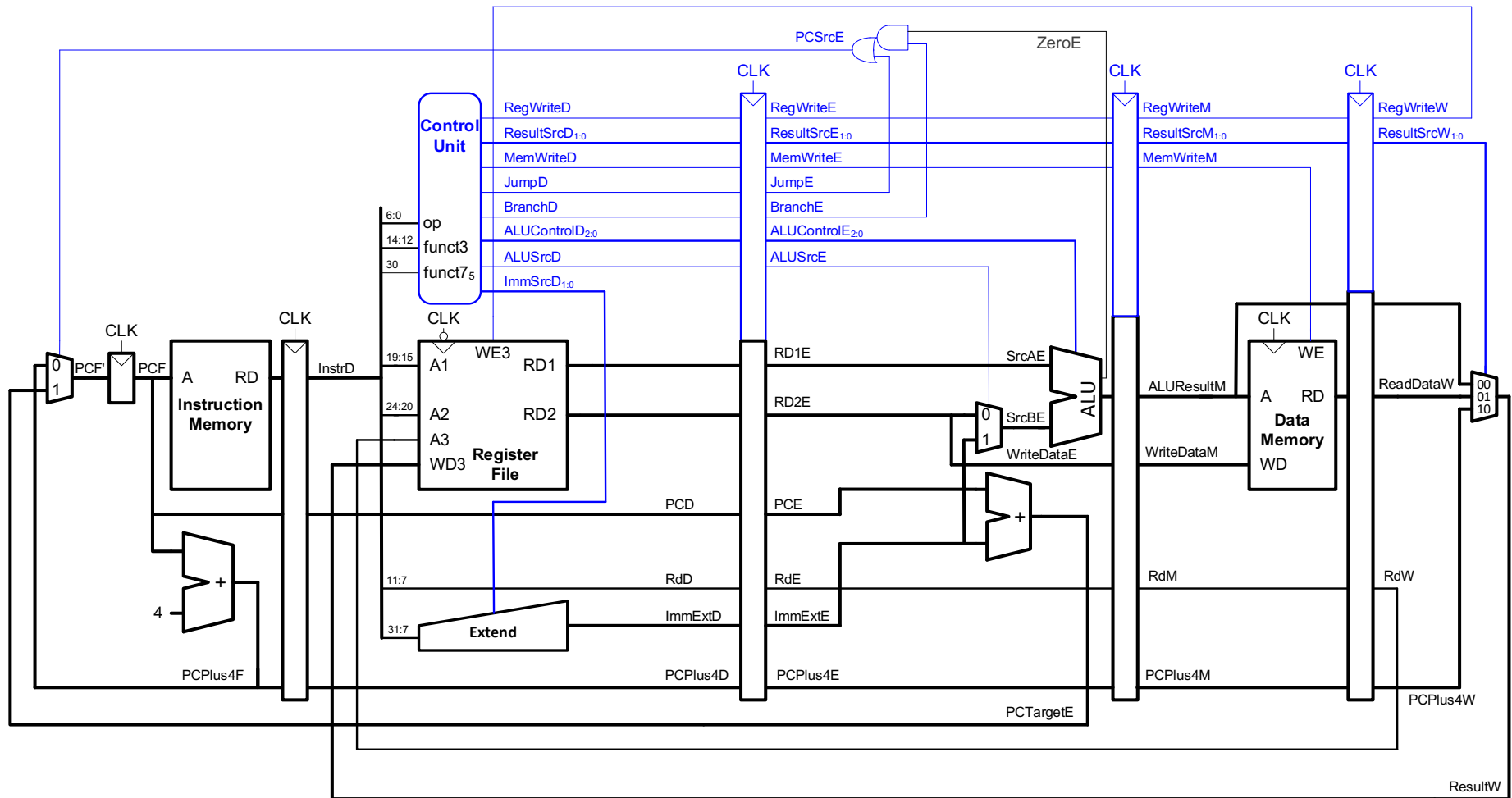

- **Same control unit** as single-cycle processor
- **Control signals travel with** the instruction (drop off when used)


# **Pipelined Processor Hazards**



# Pipelined Hazards


- When an instruction depends on result from instruction that hasn't completed
- Types:
  - **Data hazard:** register value not yet written back to register file
  - **Control hazard:** next instruction not decided yet (caused by branch)

# Data Hazard

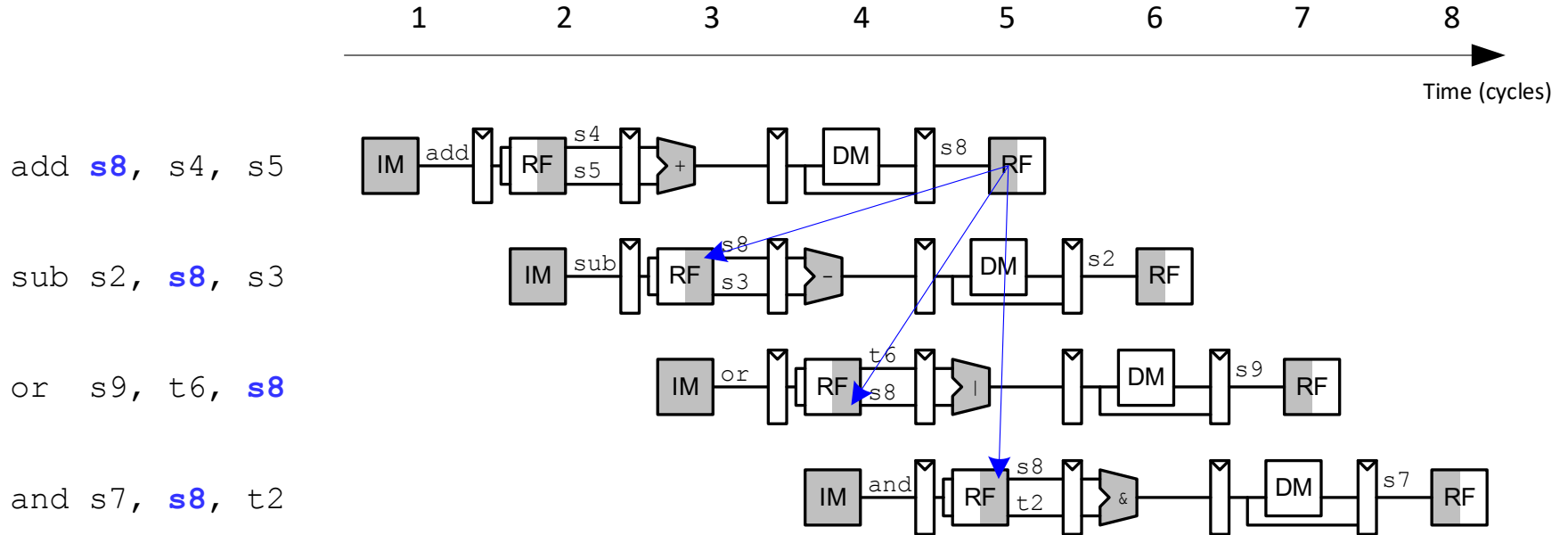

 
# Handling Data Hazards

- **Insert** enough **nops** for result to be ready
- Or move independent useful instructions forward



 
# Data Forwarding

- Data is **available on internal busses** before it is written back to the register file (RF).
- **Forward data** from internal busses **to Execute stage**.



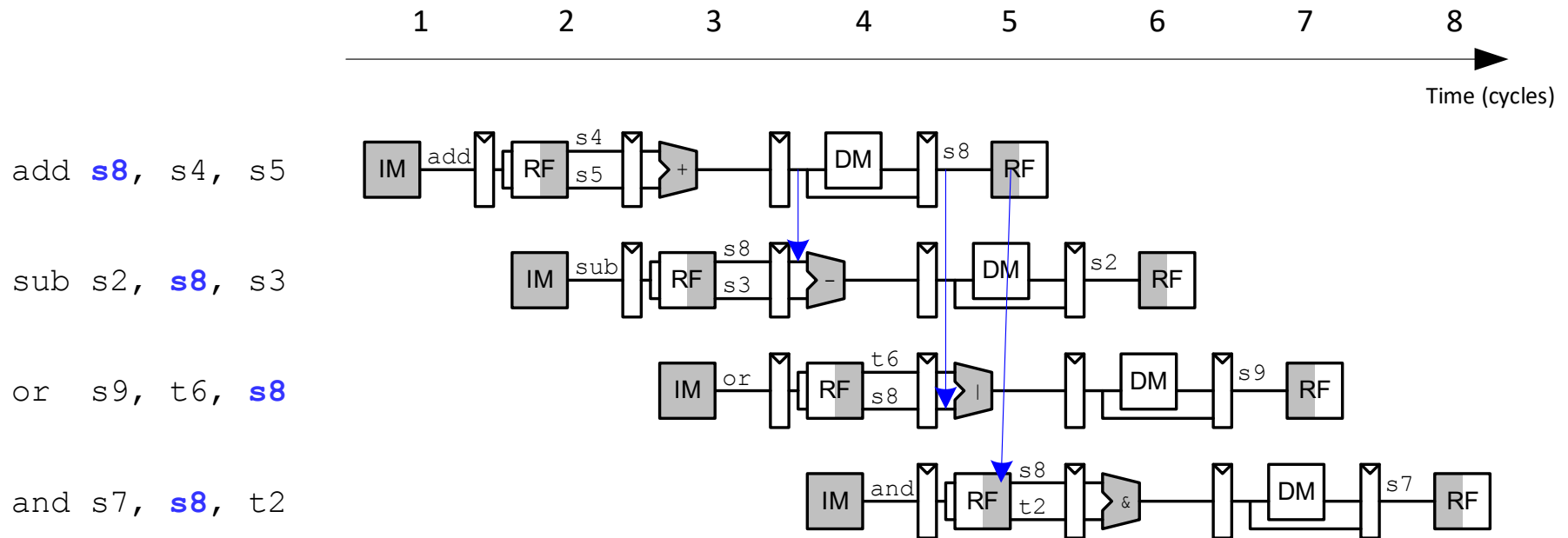
# Data Forwarding

- Check if source register **in Execute stage matches** destination register of instruction **in Memory or Writeback stage**.
- If so, forward result.



# Data Forwarding: Hazard Unit

 

# Data Forwarding

- **Case 1:** **Execute** stage  $Rs1$  or  $Rs2$  matches **Memory** stage  $Rd$ ?  
Forward from Memory stage
- **Case 2:** **Execute** stage  $Rs1$  or  $Rs2$  matches **Writeback** stage  $Rd$ ?  
Forward from Writeback stage
- **Case 3:** Otherwise use value read from register file (as usual)

Equations for  $Rs1$ :

```
if      (( $Rs1E == RdM$ ) AND  $RegWriteM$ )           // Case 1
         $ForwardAE = 10$ 
else if (( $Rs1E == RdW$ ) AND  $RegWriteW$ )           // Case 2
         $ForwardAE = 01$ 
else     $ForwardAE = 00$                            // Case 3
```

***ForwardBE** equations are similar (replace  $Rs1E$  with  $Rs2E$ )*

# Data Forwarding

- **Case 1:** **Execute** stage  $Rs1$  or  $Rs2$  matches **Memory** stage  $Rd$ ?  
Forward from Memory stage
- **Case 2:** **Execute** stage  $Rs1$  or  $Rs2$  matches **Writeback** stage  $Rd$ ?  
Forward from Writeback stage
- **Case 3:** Otherwise use value read from register file (as usual)


Equations for  $Rs1$ :

```
if      (( $Rs1E == RdM$ ) AND  $RegWriteM$ ) AND ( $Rs1E != 0$ ) // Case 1
        ForwardAE = 10
else if (( $Rs1E == RdW$ ) AND  $RegWriteW$ ) AND ( $Rs1E != 0$ ) // Case 2
        ForwardAE = 01
else    ForwardAE = 00                                     // Case 3
```


*ForwardBE equations are similar (replace  $Rs1E$  with  $Rs2E$ )*



# Data Hazard due to lw Dependency

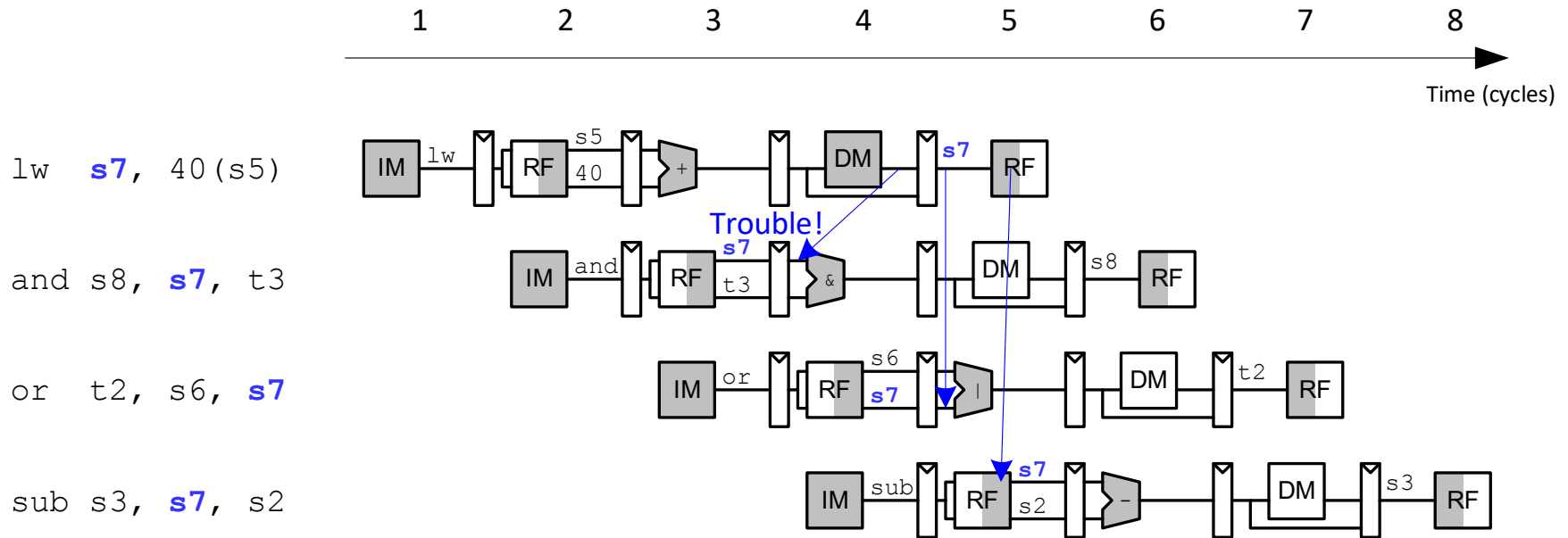

# Stalling to solve 1w Data Dependency

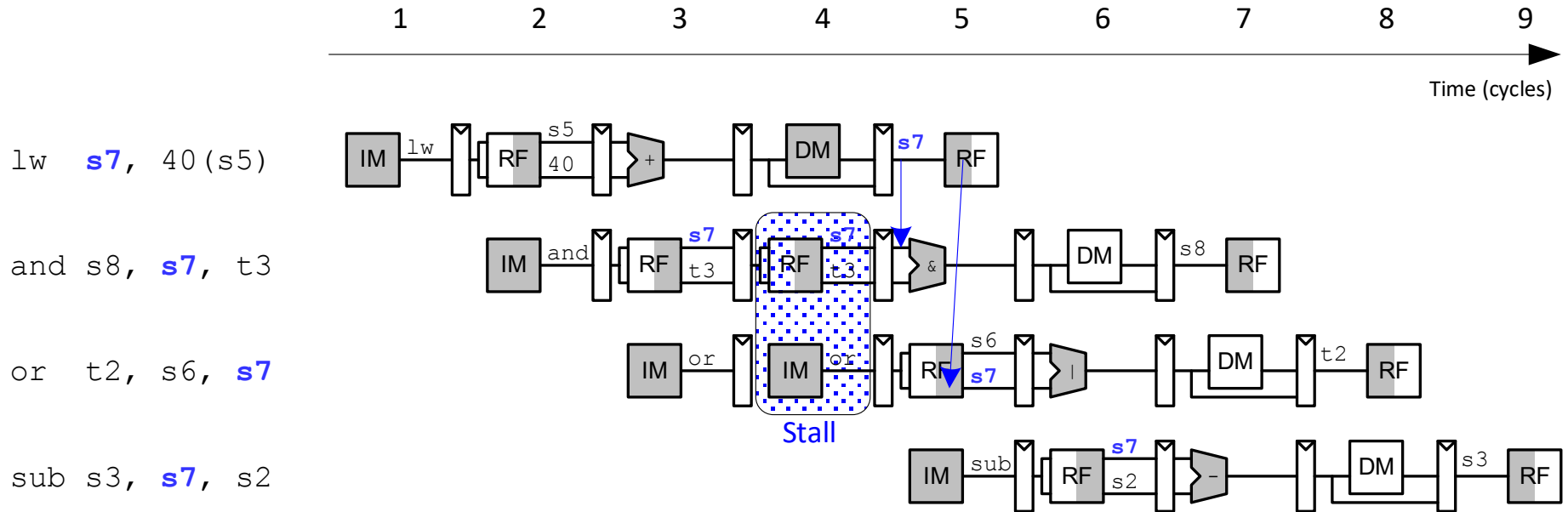

# Stalling Logic

- Is either **source register in the Decode stage** the same as the **destination register in the Execute stage**?

**AND**


- Is the instruction in the **Execute stage a lw**?

$lwStall = ((Rs1D == RdE) \text{ OR } (Rs2D == RdE)) \text{ AND } ResultSrcE_0$

$StallF = StallD = FlushE = lwStall$

(Stall the Fetch and Decode stages, and flush the Execute stage.)

# Stalling Hardware

 


# **Pipelined Processor Control Hazards**

# Control Hazards

- **beq:**
  - Branch **not determined until the Execute stage** of pipeline
  - **Instructions** after branch **fetch** before branch occurs
  - These **2 instructions must be flushed** if branch happens

# Control Hazards

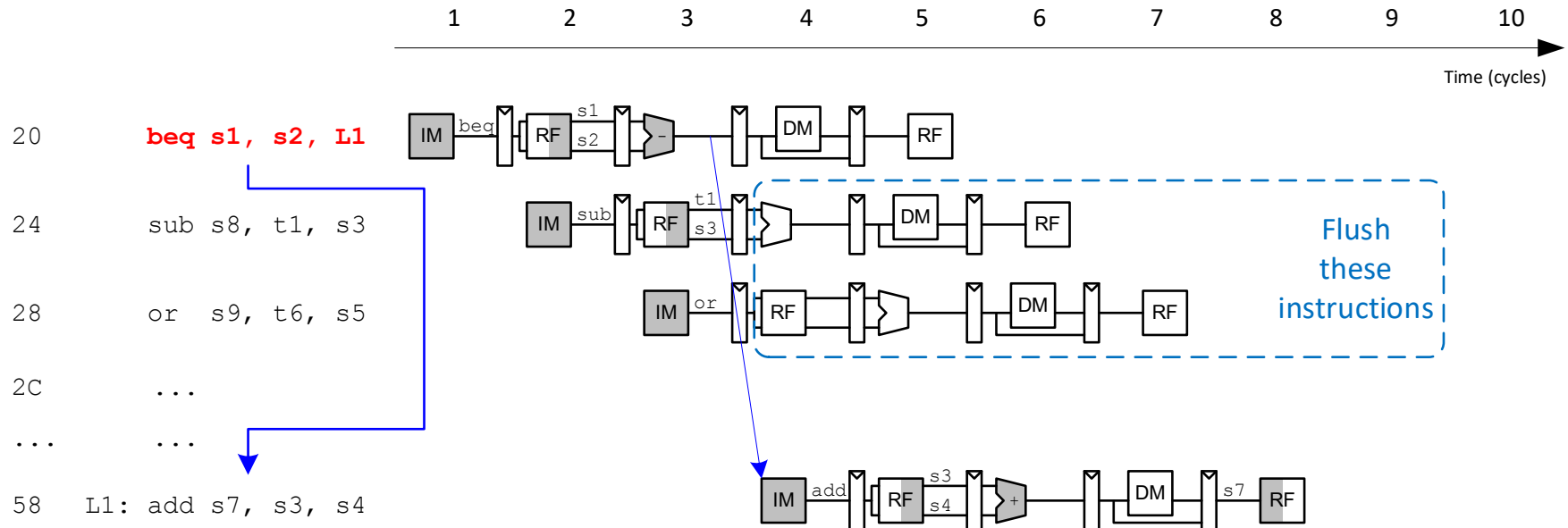

## Branch misprediction penalty:

The number of instructions flushed when a branch is taken (in this case, 2 instructions)

# Control Hazards: Flushing Logic


- If branch is taken in execute stage, need to flush the instructions in the Fetch and Decode stages
  - Do this by clearing Decode and Execute Pipeline registers using *FlushD* and *FlushE*
- **Equations:**

$$FlushD = PCSrcE$$


$$FlushE = lwStall \text{ OR } PCSrcE$$



# Control Hazards: Flushing Hardware

 
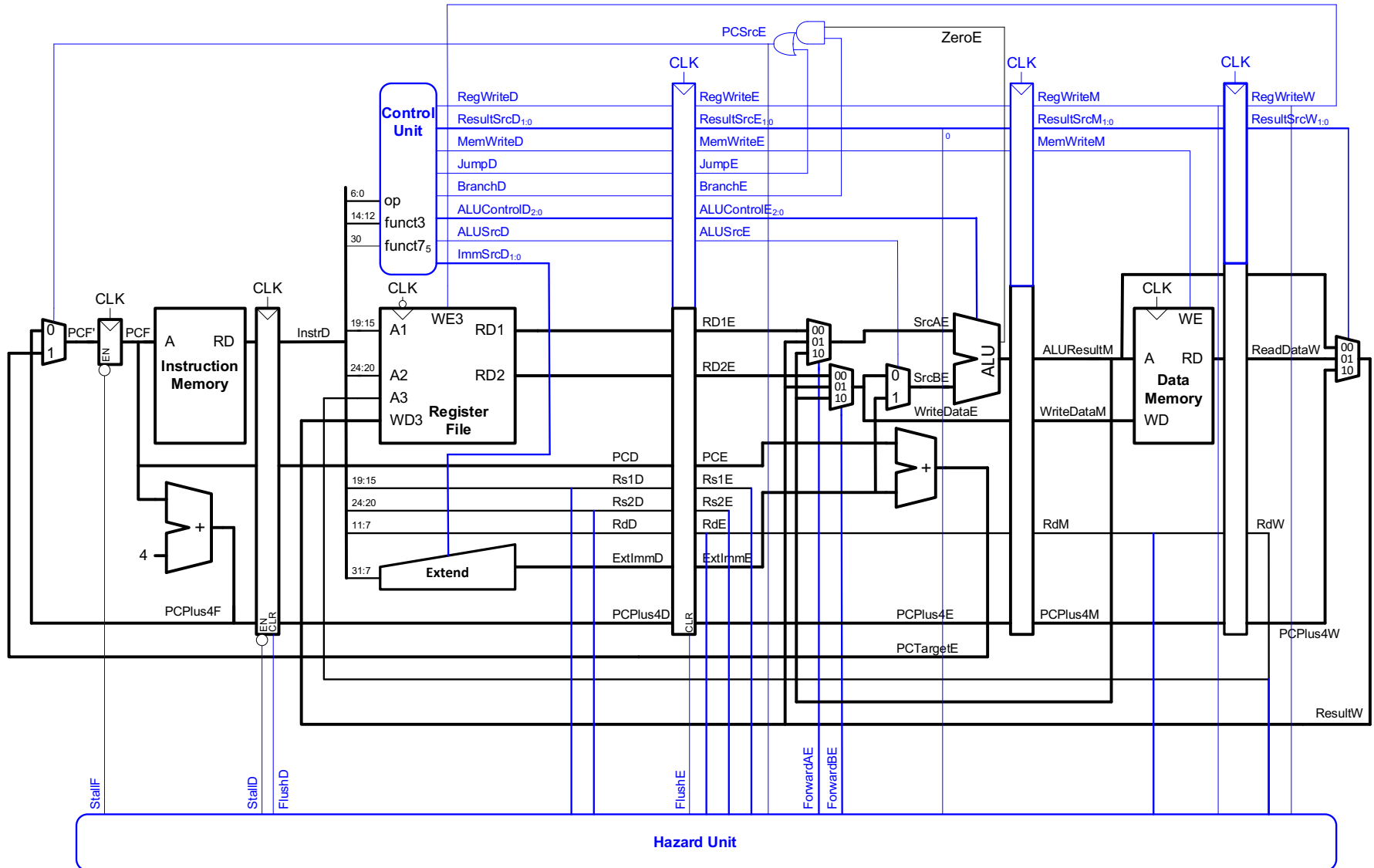
# RISC-V Pipelined Processor with Hazard Unit



# Summary of Hazard Logic

## Data hazard logic (shown for SrcA of ALU):

```
if      ((Rs1E == RdM) AND RegWriteM) AND (Rs1E != 0)    // Case 1
        ForwardAE = 10
else if ((Rs1E == RdW) AND RegWriteW) AND (Rs1E != 0)    // Case 2
        ForwardAE = 01
else    ForwardAE = 00                                     // Case 3
```

## Load word stall logic:

```
lwStall = ((Rs1D == RdE) OR (Rs2D == RdE)) AND ResultSrcE0
StallF = StallD = lwStall
```

## Control hazard flush:

```
FlushD = PCSrcE
FlushE = lwStall OR PCSrcE
```